
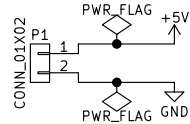


Power supply  
modified USB cable

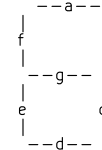



**! WARNING !**  
This circuit is not physically checked  
it would be a pain to put all on  
breadboard but a perfboard might  
be a relatively ok

This is a diode ROM  
similar that was used in pioneers of  
computing. Look up "diode matrix"



	abcdeg
1	0110000
2	1101101
3	1111001
4	0110011
5	1011011
6	1011111
7	1110000
8	1111111
9	1111011
0	1111110

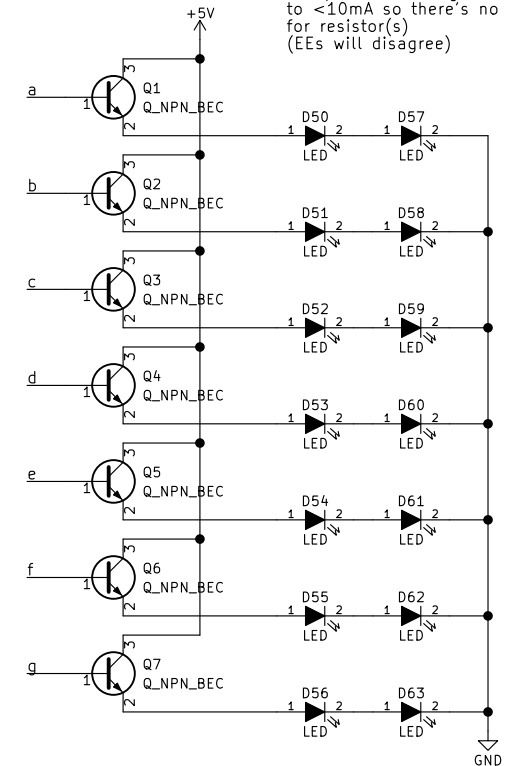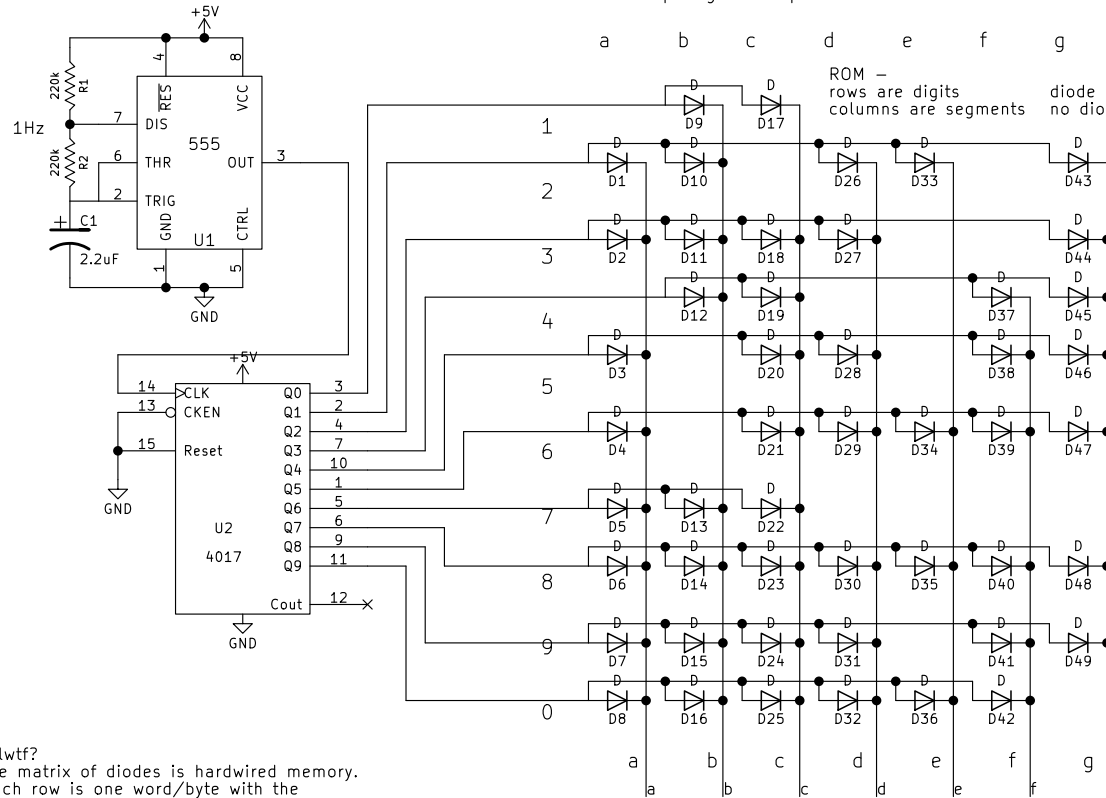Single digit  
7 segment display  
from discrete LEDs  
The power is voltage-limited  
to <10mA so there's no need  
for resistor(s)  
(EEs will disagree)



Q: lolwtf?

A: The matrix of diodes is hardwired memory.  
Each row is one word/byte with the  
length of 7 bits. The circuit 'stores' data  
for displaying a number on a 7 segment LED display  
(hence 7 bit word)  
I'll be making the memory and the display from  
discrete diodes and the only chips are for  
changing the address. Counting up at 1Hz frequency.  
It would also work by putting logic HIGH on anode  
of one of the leftmost diodes and get your output  
on the bottom. That's where the display is wired.

Sheet: /  
File: discrete7segment.sch

**Title: Discrete ROM 7-segment driver**

Size: A4 Date: 2018-04-21

KiCad E.D.A. kicad 4.0.5+dfsg1-4

Rev:

Id: 1/1